

EES4725

Digital Circuits and

FPGA Design

Chua Dingjuan
elechuad@nus.edu.sg

Lecture 3

VERILOG FOR COMBINATIONAL LOGIC

DATAFLOW – ASSIGN

BEHAVIOURAL – ALWAYS @ (*)

STRUCTURAL - INSTANTIATION

Recall where we last left off....


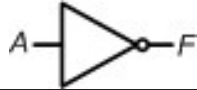


```
module box(input  a, b,
           input  [1:0] c,
           output [3:0] y );
```

```
wire tmp;
reg [1:0] one = 3;
reg two;
integer three = 1;
```

```
assign y[3] = one[0];
assign y[2:1] = a + c;
assign y[0] = ( a > b );
```

```
endmodule
```

Net / Variable Name	Number of bits?	Value in dec / bin
a	1	1 / 1'b1
b	1	0 / 1'b0
c	2	2 / 2'b10
tmp	1	Z / 1'bZ
one	2	3 / 2'b11
two	1	X / 1'bX
three	32	1 / 32'h00000001
y	4	15 / 4'b1111


Gate	Symbol	Function (F)	Verilog Operator	Gate	Symbol	Function (F)	Verilog Operator
AND		$A \cdot B$	$F = A \& B$	NOT		\bar{A}	$F = \sim A$
OR		$A + B$	$F = A B$	XOR		$A \oplus B$	$F = A \wedge B$

```
assign F = ~w & ~x & z | ~w & x & z | w & y & z | x & y & z;
```


Design Workflow!




RTL Schematic

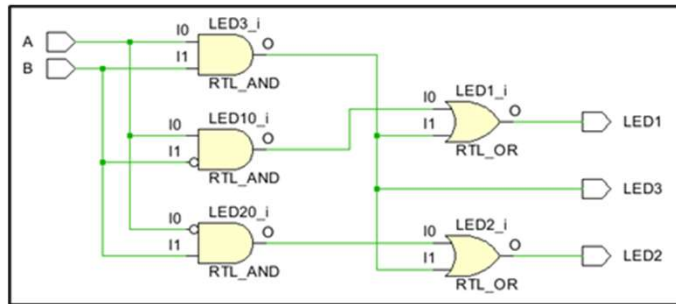

Synthesized Schematic

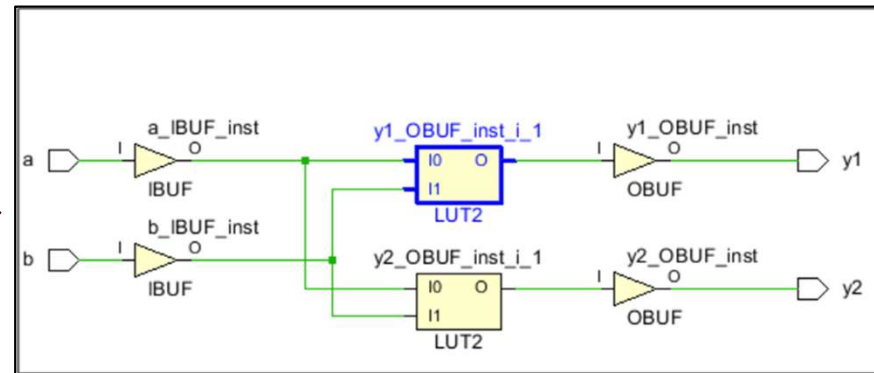


Simulation Results

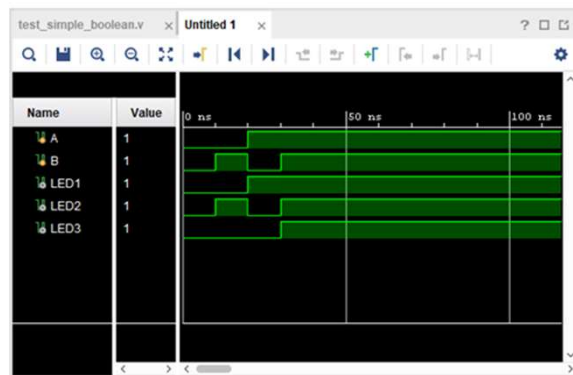

.xdc (Constraints Mapping)

```
Project Summary | my_basys3_constraints.xdc |  
C:\Users\Christopher\Desktop\Lab_1\Lab_1\src\constrs_1\newmy_basys3_constraints.xdc  
10  
11 ## Switches  
12 set_property -dict { PACKAGE_PIN V17 IOSTANDARD LVCMOS33 } [get_ports { A }]  
13 set_property -dict { PACKAGE_PIN V16 IOSTANDARD LVCMOS33 } [get_ports { B }]  
14 set_property -dict { PACKAGE_PIN W16 IOSTANDARD LVCMOS33 } [get_ports { sw[2] }]  
15 set_property -dict { PACKAGE_PIN W17 IOSTANDARD LVCMOS33 } [get_ports { sw[3] }]  
16 set_property -dict { PACKAGE_PIN W18 IOSTANDARD LVCMOS33 } [get_ports { sw[4] }]  
17 set_property -dict { PACKAGE_PIN W19 IOSTANDARD LVCMOS33 } [get_ports { sw[5] }]  
18 set_property -dict { PACKAGE_PIN W14 IOSTANDARD LVCMOS33 } [get_ports { sw[6] }]  
19 set_property -dict { PACKAGE_PIN W15 IOSTANDARD LVCMOS33 } [get_ports { sw[7] }]  
20 set_property -dict { PACKAGE_PIN V0 IOSTANDARD LVCMOS33 } [get_ports { sw[8] }]  
21 set_property -dict { PACKAGE_PIN T3 IOSTANDARD LVCMOS33 } [get_ports { sw[9] }]  
22 set_property -dict { PACKAGE_PIN T2 IOSTANDARD LVCMOS33 } [get_ports { sw[10] }]  
23 set_property -dict { PACKAGE_PIN R3 IOSTANDARD LVCMOS33 } [get_ports { sw[11] }]  
24 set_property -dict { PACKAGE_PIN R2 IOSTANDARD LVCMOS33 } [get_ports { sw[12] }]  
25 set_property -dict { PACKAGE_PIN U1 IOSTANDARD LVCMOS33 } [get_ports { sw[13] }]  
26 set_property -dict { PACKAGE_PIN T1 IOSTANDARD LVCMOS33 } [get_ports { sw[14] }]  
27 set_property -dict { PACKAGE_PIN R2 IOSTANDARD LVCMOS33 } [get_ports { sw[15] }]  
28
```

.bit (Bitstream)

 

Is this OK?

```
module notgood
(input a,b, output x, y);


  reg z;  always
  assign z = a | b;

endmodule
```



Continuous Assignment (Dataflow)

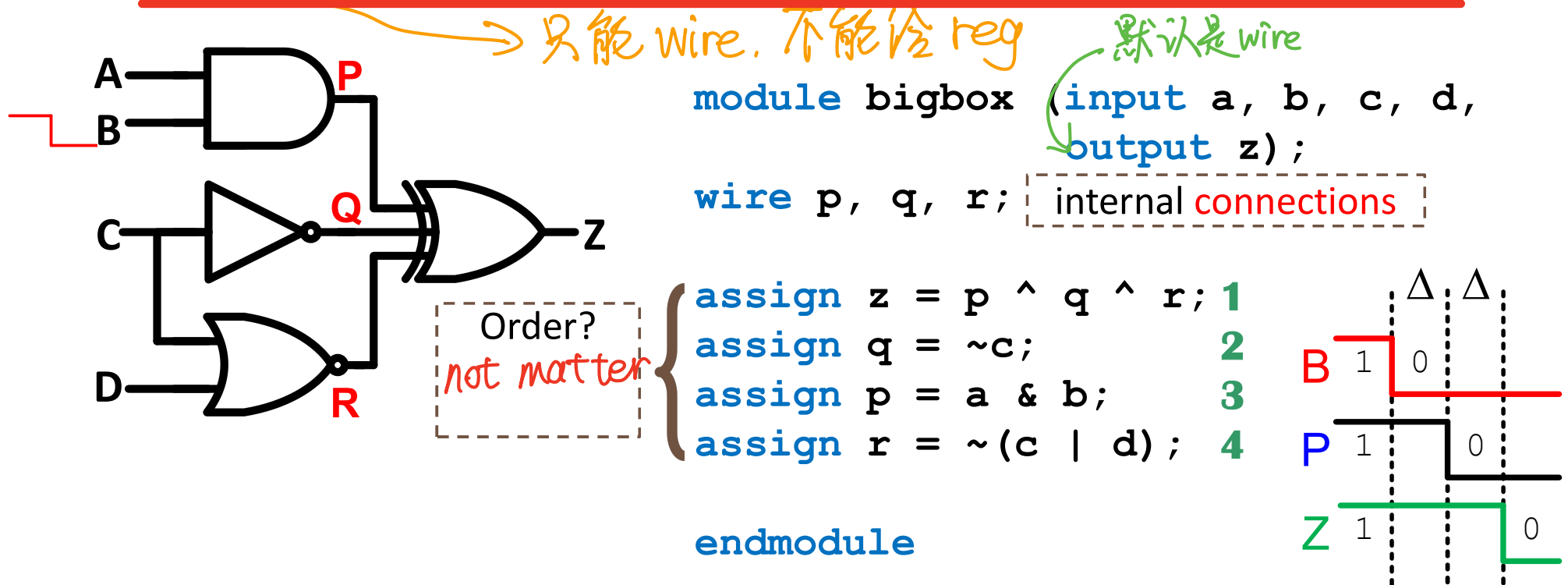assign statements are often used to model combinational logic



- Whenever there's an **event** on the RHS signal, expression is evaluated and assigned (Δ) \rightarrow *continuously monitored*
- Multiple statements can be executed in parallel (concurrently) 并行地
- **wire** is used to represent an internal connection

Is this OK?

```
module notgood(...);
```

```
    assign x = a | b;
```

```
    assign x = a + b;
```

```
endmodule
```


两个输入 → 可能短路



Implementation (2 errors)

- Opt Design (2 errors)
 - DRC (1 error)
 - Netlist (1 error)
 - Net (1 error)
 - [DRC MDRV-1] Multiple Driver Nets: Net x_OBUF has multiple drivers: x_OBUF_inst_i_1/O, and x_OBUF_inst_i_2/O.
- [Vivado_Tcl 4-78] Error(s) found during DRC. Opt_design not run.

Useful Operators

 


- Boolean (bit-wise), logical, arithmetic, concatenation.
- Use brackets for readability, take note if **synthesizable*.

Precedence ↑ High ↓ Low	Operator	Description	Examples: a = 4'b1010, b=4'b0000
	!, ~	Logical negation, Bit-wise NOT	!a = 0, !b = 1, ~a=4'b0101, ~b=4'b1111
	&, , ^	Reduction (Outputs 1-bit)	&a = 0, a=1, ^a = 0 自己从第1位开始, 逐位运算 &a = 1&0&1&0
	{ __, __ }	Concatenation	{b, a} = 8'b00001010
	{n{ __ } }	Replication	{2 {a}} = 8'b10101010
	*, /, %	Multiply, *Divide, *Modulus	3 % 2 = 1, 16 % 4 = 0
	+, -	Binary addition, subtraction	a + b = 4'b1010
	<<, >>	Shift Zeros in Left / Right	a << 1 = 4'b0100, a >> 2 = 4'b0010
	<, <=, >, >=	Logical Relative (1-bit output)	(a > b) = 1
	==, !=	Logical Equality (1-bit output)	(a == b) = 0 (a != b) = 1
	&, ^,	Bit-wise AND, XOR, OR	a&b = 4'b0000 a b = 4'b1010
	&&,	Logical AND, OR (1-bit output)	a&&b = 0 a b = 1
	?:	Conditional Operator	<out> = <condition> ? If_ONE : if_ZERO

Conditional Operator...

 The `?:` conditional operator allows us to select the output from a set of inputs based on a condition.



```
module mystery ( input s, input [1:0] d,  
                 output y );
```

```
assign y = s ? d[1] : d[0];
```


`<output> = <condition> ? If_ONE : If_ZERO`

`s = 1 → y = d[1], s = 0 → y = d[0]`

```
endmodule
```

- This expression is evaluated whenever there is an event on any input.
- What is this block? *-2-1 Multiplexer → MUXI*

Write the code for 4-1 MUX

 

Lecture 3

Exercise


Q1

Procedural Assignment : **always**

Behavioral, higher-level description of logic.

2 assignment types : **Blocking & Non-Blocking**
 
```
module mux21 (input s, input d[1:0],
              output reg y);
```



Anything assigned in an **always** block must be declared as type **reg**

always @ { * (all inputs) (s, d)

```
begin
  if (sel == 1'b0)
    y = d[0];
  else
    y = d[1];
end
```

Conceptually, the **always** block runs once when any signal in **sensitivity list** (s,d) changes value.

Statements executed sequentially & evaluated instantaneously. → Order matters!

begin and **end** behave like parentheses/brackets for conditional statements.

```
end
endmodule
```

Some notes on: `always`

- `always@(*)` includes all signals that are read in statements.
- Statements within `always` block are executed *sequentially*.
- Variables within sensitivity list are very important!
- `if--else if--else, case, for, while` can only be used in procedural assignments (always blocks)
- Multiple always blocks run in parallel, concurrently, watch out for multi-driven nets and race conditions. (next slide)
- No ~~`assign`~~ in always blocks!

Registers

- Anything assigned in an `always` block must be declared as type `reg`
- In Verilog, the term register (`reg`) simply means a variable that can hold a value. (cf. `wire`)

↓ 寄存器:

- 1) 有无 `posedge/negedge`
- 2) 有无 `clock`
- 3) 有无记忆行为

Is this OK?

```
module notgood(...);  
    always @ (*)  
        y = y + 1;  
  
    always @ (*)  
        y = y + 3;  
  
endmodule
```

Ref – Conditional Statements

If - else if - else

```
if ( expr )  
    statement;
```

```
if ( expr )  
    statement;  
else  
    statement;
```


```
if ( expr )  
    statement;  
else if ( expr )  
    statement;  
else if ( expr )  
    statement;  
else  
    statement;
```

case

```
case ( expr )  
  
    value1 : statement;  
    value2 : statement;  
    value3 : statement;  
    ...  
    default : statement;  
  
endcase
```


Equivalence
 
```
module mux21 ( input s, input [1:0] d, output reg y);  
  
always @ (s, d)  
begin  
    if (s == 1'b0)  
        y= d[0];  
    else  
        y= d[1];  
end  
endmodule
```



```
module mux ( input s, input [1:0] d, output y);  
  
assign y = s ? d[1] : d[0];  
  
endmodule
```

Equivalence...

 

```
module bigbox
(input a,b,c,d, output z);
```

```
wire p, q, r;
```

```
assign q = ~c;
assign z = p ^ q ^ r;
assign p = a & b;
assign r = ~(c | d);
```

```
endmodule
```

```
module bigbox
(input a,b,c,d, output reg z);
  reg p,q,r
  always @ (a,b,c,d) /*
```

```
begin
  q = ~c;
  z = p ^ q ^ r;
  p = a & b;
  r = ~(c | d);
```

```
end
```

```
endmodule
```


最后一行

Lecture 3 Exercise Q2

Structural Modeling – Primitives

Structural modeling can be used to connect multiple modules and gates.

 Verilog provides a standard set of primitive such as basic logic gates.



Dataflow

```
module bigbox (input a,b,c,d, output z);  
    assign z = (a & b) ^ ~c ^ ~(c | d) ;  
endmodule
```


Structural (using primitives)

```
module bigbox (input a,b,c,d, output z);  
    wire p, q, r;  
  
    and u1 (p, a, b); //output, then inputs  
    not u2 (      );  
    nor u3 (      );  
    xor u4 (      );  
  
endmodule
```


Structural Modeling

Structural modeling can be used to connect multiple modules via port connection by name and position.
 
```
module mux21( input s,  
              input [1:0] d,  
              output y);  
  
    assign y = s ? d[1] : d[0];  
  
endmodule
```



 
```
module mux41( input [1:0] s,  
              input [3:0] d,  
              output y);  
  
    ... .. ?  
  
endmodule
```




Structural Modeling

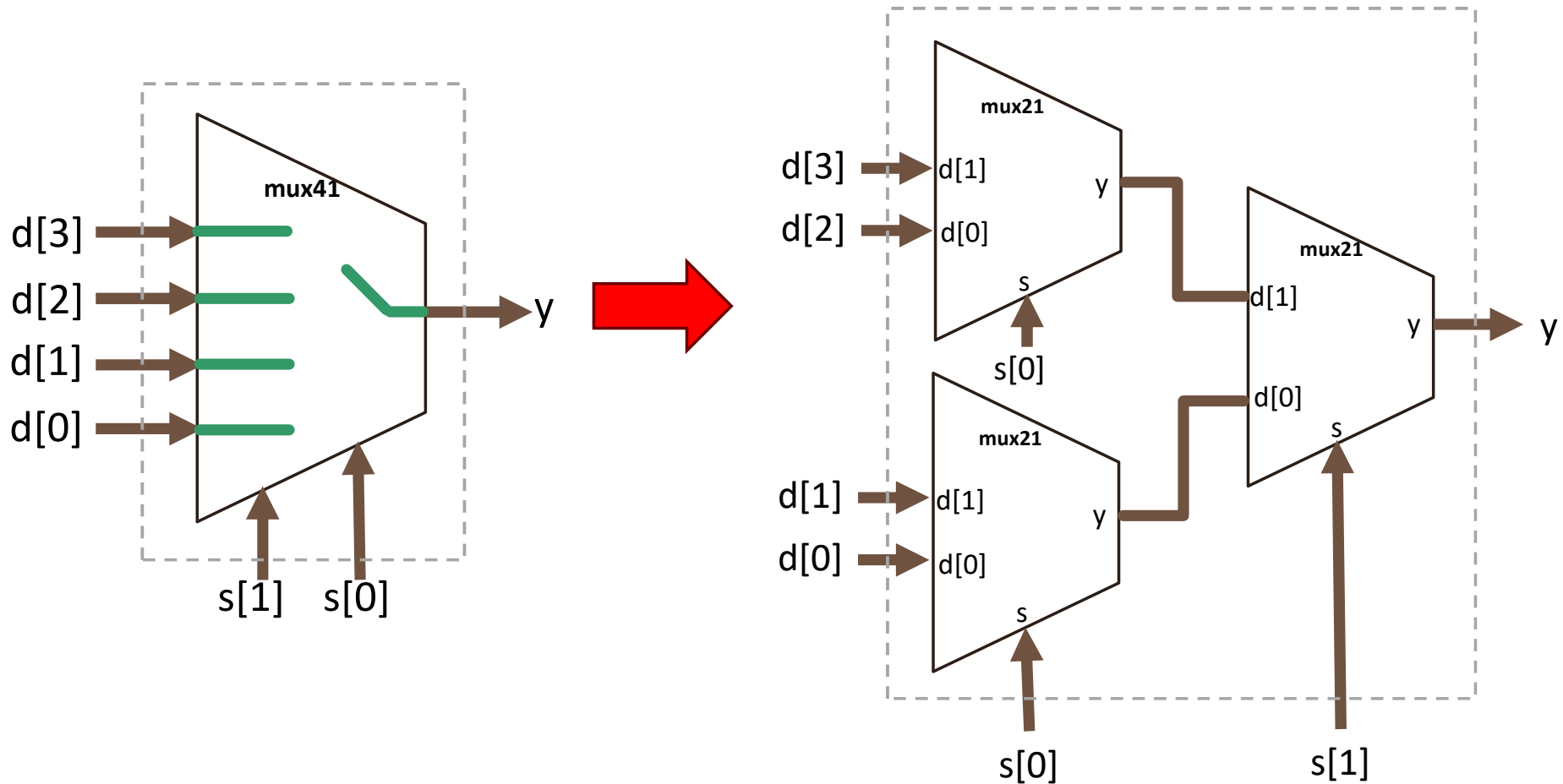For example, a 4-to-1 multiplexer can also be implemented by combining several 2-to-1 multiplexers. How can we write this in Verilog?



Structural Modeling

 For example, a 4-to-1 multiplexer can also be implemented by combining several 2-to-1 multiplexers.



```
module mux21( input s, input [1:0] d,
              output y);
    assign y = s ? d[1] : d[0];
endmodule
```

Port Connection by Position

```
module mux41( input [1:0] s,
              input [3:0] d,
              output y);

    wire out1, out2;

    //check for port order!
    mux21 u1 (s[0], d[3:2], out1);


    mux21 u2 (s[0], d[1:0], out2);

    mux21 u3 (s[1], out1, out2);

endmodule
```

Structural Modeling

 For example, a 4-to-1 multiplexer can also be implemented by combining several 2-to-1 multiplexers.



Port Connection by Name

```
module mux41( input [1:0] s,
              input [3:0] d,
              output y);

  wire out1, out2;

  mux21 u1 (.s (s[0]),
            .d (d[3:2]),
            .y (out1));

  mux21 u2 (.s
            .d
            .y
            );


  mux21 u3 (.s (s[1]),
            .d (out1, out2),
            .y (y));

endmodule
```

Structural Modeling

- For modular designs, the top design is often specified as interconnected blocks.
- Two examples below demonstrate port connection by position / name.
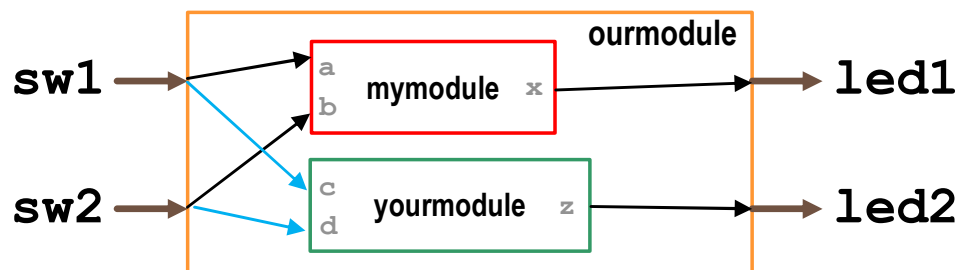
```
module mymodule (input a, b, output x);  
...  
endmodule
```



Port Connection by Position

```
module ourmodule (input sw1, sw2,  
                  output led1, led2);  
  
mymodule M1 (sw1, sw2, led1);  
yourmodule M2 (sw1, sw2, led2);  
  
endmodule
```

```
module yourmodule (input c, d, output z);  
...  
endmodule
```


Port Connection by Name

```
module ourmodule (input sw1, sw2,  
                  output led1, led2);  
  
mymodule M1 ( .a (sw1),  
              .b (sw2),  
              .x (led1) );  
  
yourmodule M2 ( .z(led2),  
               .c (sw1),  
               .d(sw2) );  
  
endmodule
```

Recall Simulation?


 
```
module savetheworld (input a1, ... z1,  
                     output a2, ..., z2) ;  
    .....  
    .....  
    .....  
endmodule
```



How do we know our design actually works?

- Functional Simulation
(Xilinx)

Method


- Designer applies input values to the code
- Simulator produces corresponding outputs in truth tables / timing diagrams
- Simulators usually assume negligible propagation gate delays.

Verilog Code

```
module  
    .....  
    .....  
endmodule
```

Test Bench
 
```
call module  
a1=9;  
b1=1;  
//wait for 10u  
#10  
b1=0;
```



可忽略的

Simulation Testbench Example

```
module mux21( input s,  
              input [1:0] d,  
              output y);  
    assign y = s ? d[1] : d[0];  
endmodule
```

```
module mux_test();
```

```
    reg [1:0] ip = 0;
```

```
    reg sel = 0;
```

```
    wire op;
```

```
    mux21 dut (sel, ip, op);
```

```
    initial begin
```



```
        ip = 2'b10;
```

```
        sel = 1'b0;
```

```
        #10; //wait 10 time units
```

```
    end
```

```
endmodule
```

  

Pre-Lab Preparation Q3
