

# **EES4725**

# **Digital Circuits and FPGA Design**

---

Chua Dingjuan  
elechuad@nus.edu.sg


# Lecture 4

A thick red horizontal bar that starts under the 'L' of 'Lecture' and extends to the right, ending under the '4'.

SEQUENTIAL LOGIC - JK, D, T FLIP-FLOPS

VERILOG FOR SEQUENTIAL LOGIC

# Design a logic circuit to do this >>

 


When the button is pushed :

- 1) Turn On the light *if* it is Off
- 2) Turn Off the light *if* it is On



*What is missing?*

 
- 1) Remembering the previous state of the bulb → **MEMORY**
- 2) Responding to an input **EVENT** (cf. input value)



# Sequential Logic Circuits?

## Combinational Logic Circuits:

- Outputs depend on current inputs

 


## Sequential Logic Circuits:

- Outputs depend on **current and previous** inputs → Memory!
- Requires separation of previous, current, future : **states**
- 2 Types of sequential circuits:

Synchronous	Asynchronous
Clocked: need a clock input	Unclocked
Responds to inputs at discrete time instants governed by a clock input	Responds whenever input signals change



# JK Flip Flop

 

The universal JK flip flop is a commonly used flip flop in digital circuits.

CLK	J	K	Q+
↑	0	0	Q
↑	0	1	0
↑	1	0	1
↑	1	1	$\bar{Q}$

condensed characteristic table


Hold  
Clear  
Set  
Toggle

CLK	J	K	Q	Q+
↑	0	0	0	0
↑	0	0	1	1
↑	0	1	0	0
↑	0	1	1	0
↑	1	0	0	1
↑	1	0	1	1
↑	1	1	0	1
↑	1	1	1	0

characteristic table


The JK FF is a **synchronous** circuit:

 - Clock input* is a controlling input.  
It specifies when circuit read inputs / change outputs.
- Synchronous circuits* respond only at the **active** clock edges  
i.e., **LOW** → **HIGH**, **HIGH** → **LOW** transitions




- At any other time, changing inputs have no effect on the output.

# Respond @ Active Clock Edges

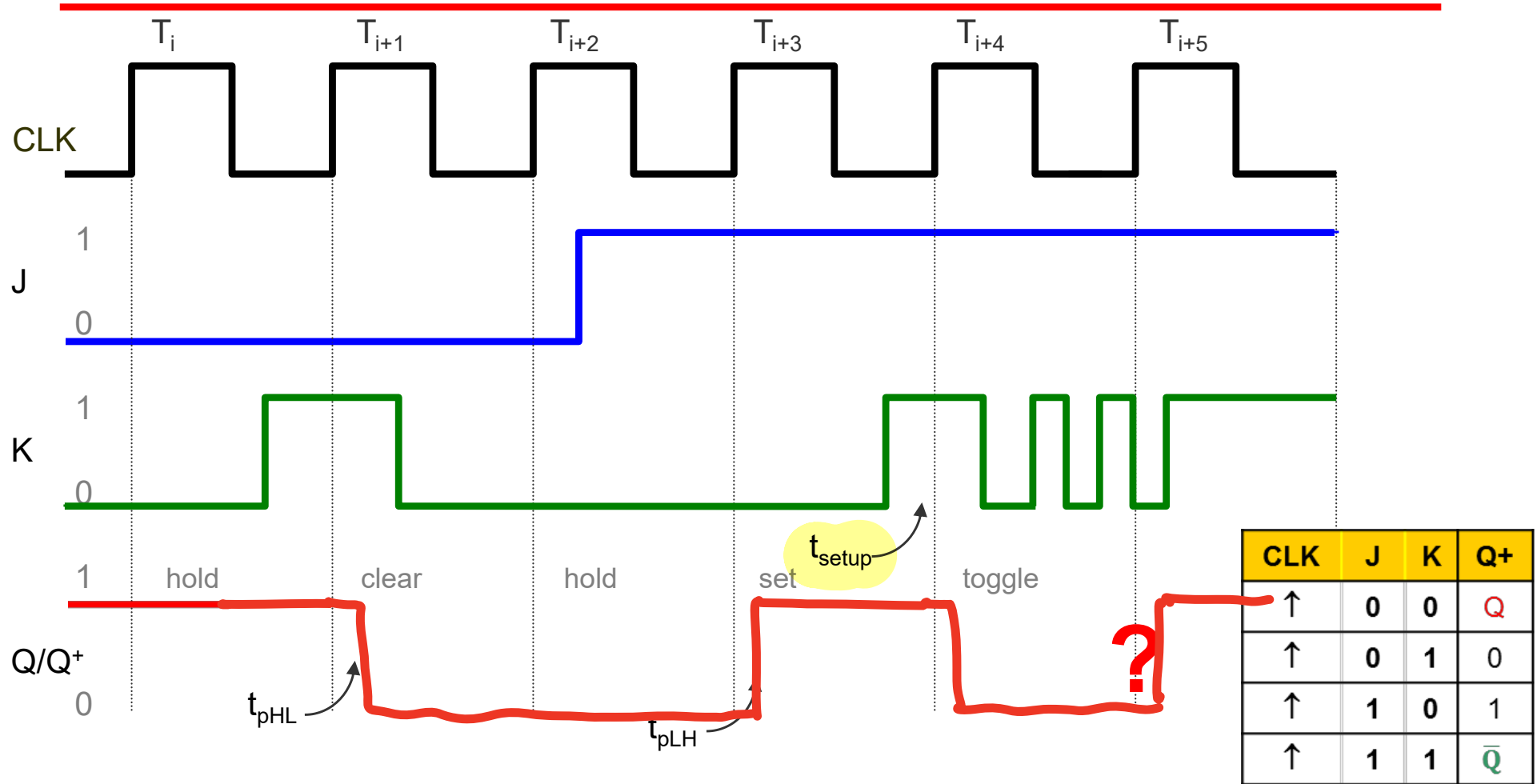

- When inputs don't change → FF outputs don't change.
- If inputs change → FF output changes state only at active clock edge.

# FF Timing Parameters

 

$t_{setup}$  :

minimum time before the *active* clock edge by which FF inputs must be stable.

$t_{hold}$  :

minimum time inputs must be stable after *active* clock edge

$t_{pHL}$  :

time taken for FF output to change state from **High** to **Low**.

$t_{pLH}$  :

time taken for FF output to change state from **Low** to **High**.

What happens if inputs change state right at the active clock transition?

Answer: output is unpredictable

Thus, input changes must meet required **setup** & **hold** times of device  
== Operating Speed of device

## ◆ t\_setup (建立时间)

- 含义：

在“有效时钟边沿到来之前”，输入必须已经稳定的最短时间

- 直觉理解：

👉 别等铃响才交卷，得提前交

- 若违反：

FF 来不及“看清”输入，可能采样错误

---

## ◆ t\_hold (保持时间)

- 含义：

在“有效时钟边沿之后”，输入仍需保持不变的<sup>最短</sup>时间

- 直觉理解：

👉 铃刚响完，先别立刻改答案

- 若违反：

FF 刚采样完，输入就变了，结果可能出错



# Maximum Clock Frequency

---


For a JK Flip-flop with the following parameters, what is the maximum theoretical clock speed?

$$t_{\text{setup}} = 10\text{ns}$$

$$t_{\text{pLH}} = t_{\text{pLH}} = 20\text{ns}$$


$$f_{\text{clk,max}} = \frac{10\text{ns} + 20\text{ns}}{1} = 33\text{M}$$

# Other Flip-Flops...

 


**D Flip-Flop**

CLK	D	Q <sup>+</sup>
↑	0	0
↑	1	1

 


**D Latch**

EN	D	Q <sup>+</sup>
0	X	No change
1	0	0
1	1	1

 

**T Flip-Flop**

CLK	T	Q <sup>+</sup>
↑	0	Q
↑	1	$\bar{Q}$

 

A T Flip-flop made from a J-K Flip-flop

CLK	J	K	Q <sup>+</sup>
↑	0	0	Q
↑	0	1	0
↑	1	0	1
↑	1	1	$\bar{Q}$

Since **T Flip-flops** are easy to construct from other FFs, they are not often used commercially.

## 1 Latch 是什么（一句话）

Latch（锁存器）是“电平敏感”的存储元件：

👉 只要使能信号有效，输入怎么变，输出就跟着变；失能后才“记住”最后的值。

## 2 和 Flip-Flop 的本质区别（重点）

对比点	Latch	Flip-Flop (FF)
触发方式	电平触发 (level-sensitive)	边沿触发 (edge-triggered)
何时更新	使能有效期间一直更新	仅在时钟边沿瞬间
时序分析	复杂、容易出问题	简单、可控
FPGA / 数字系统	一般不推荐用	主流选择

👉 Latch = 门没关死

👉 FF = 门只在“咔哒”一瞬间开一下

## ✗ 典型“无意中生成 latch”的代码

verilog

📄 复制

```
always @(*) begin
    if (en)
        q = d;
    // else 什么都没写
end
```

综合器理解为：

en=1 → q = d

en=0 → q 必须记住上一次的值

👉 这正是 latch 的定义

## ✅ 如果你不想要 latch，必须这样

verilog

📄 复制

```
always @(*) begin
    if (en)
        q = d;
    else
        q = 1'b0; // 或其他明确赋值
end
```

📌 always @(\*) 里：所有路径都必须赋值



# Verilog for Sequential Logic

---


# In previous labs and lectures...

---


- module
  - wire (net) , reg
  - Logic gates ( $\sim$ ,  $\&$ ,  $|$ ,  $\wedge$  )
  - Operators :  $+$ ,  $-$ ,  $?$   $:$ ,  $\{ \}$
  - assign
  - always @ (\*)
  - structural modeling
-

# Verilog Time! – D-FF


Let's start with a simple D FF!

 

CLK	D	Q+
↑	0	0
↑	1	1

 

# Verilog Time! – D-FF

 

CLK	D	Q+
↑	0	0
↑	1	1



↑ always @ (posedge *clk*)

↓ always @ (negedge *clk*)

```
module dff ( input d, clk,  
            output reg q );
```

Anything assigned in an **always** block must be declared as type **reg**

```
always @ (posedge clk)
```

```
begin
```

```
    q = d;
```

```
end
```

```
endmodule
```

Conceptually, the **always** block runs *once* when a signal in *sensitivity list* changes value.

**begin** and **end** behave like parentheses/brackets for conditional statements.



# Blocking & Non-blocking

Verilog supports two types of assignments within

**always**

**=** blocking assignment

- Sequential evaluation
- **Immediate** assignment

**always @ (\*)**

**begin**

**x = y;** 1) Evaluate y, assign result to x  
**z = ~x;** 2) Evaluate ~x, assign result to z  
**end**

Behaviour	x	y	z
Initial Condition	0	0	1
y changes	0	1	1
x = y	1	1	1
z = ~x	1	1	0

**<=** non-blocking assignment

- Sequential evaluation
- **Deferred** assignment

**always @ (\*)**

**begin**

**x <= y;** 1) Evaluate y, defer assignment  
**z <= ~x;** 2) Evaluate ~x, defer assignment  
3) Assign x and z with new values  
**end**

Behaviour	x	y	z	Deferred
Initial Condition	0	0	1	
y changes	0	1	1	
x <= y	0	1	1	x <= 1
z <= ~x	0	1	1	z <= 1
Assignment	1	1	0	

# Example

```
module example(input [2:0] A,
               output reg [2:0] V, Z, W);
```

```
always @ (A)
begin
```

```
1 V = A | 3'b001;
2 Z <= V | 3'b100;
3 W = Z;
```


```
end
endmodule
```

Behaviour	A	V	Z	W	Deferred
Initial Condition	000	001	101	000	
A changes	010	001	101	000	
Stmt 1	010	011	101	000	
Stmt 2	010	011	101	000	
Stmt 3	010	011	101	101	
Assignment	010	011	111	101	

An event occurs on **A** at simulation t :

- Stmt 1 is executed and V is assigned immediately
- Stmt 2 is executed and defer assignment to Z
- Stmt 3 is executed using old value of Z.
- Z is assigned.

# Verilog Time! – D-FF

 

CLK	D	Q+
↑	0	0
↑	1	1



↑ always @ (posedge \_\_\_\_)

↓ always @ (negedge \_\_\_\_)

```
module dff ( input d, clk,  
            output reg q);
```

```
always @ (posedge clk)
```

```
begin
```

```
q <= d;
```


or

```
q = d;
```


```
end
```

```
endmodule
```

# Two D Flip-Flops...

 


CLK	D	Q <sup>+</sup>
↑	0	0
↑	1	1

 

Assume initial outputs of FFs is '0' and D1 is '1'.

Behaviour	Q1	Q2
	0	0
After 1 <sup>st</sup> rising edge	1	0
After 2 <sup>nd</sup> rising edge	1	1

# Two D Flip-Flops... and Verilog!

 


Behaviour	Q1	Q2
	0	0
After 1 <sup>st</sup> rising edge	1	0
After 2 <sup>nd</sup> rising edge	1	1

```
always @ (posedge clk)
begin
```

```
q1 = d1;
q2 = q1;
```

```
end
```

 

```
always @ (posedge clk)
begin
```

```
q1 <= d1;
q2 <= q1;
```

```
end
```

*Handwritten red text: / q2 = q1*

Behaviour	Q1	Q2
	0	0
After 1 <sup>st</sup> rising edge	1	1
After 2 <sup>nd</sup> rising edge	1	1

Behaviour	Q1	Q2
	0	0
After 1 <sup>st</sup> rising edge	1	0
After 2 <sup>nd</sup> rising edge	1	1

# FFs on Artix-7 FPGA

---


# D Flip-Flop... in Vivado?

## Verilog Code


```
module dff1 (input d,clk,
output reg q);

always @ (posedge clk)
begin
q <= d;
end
endmodule
```

## Vivado RTL Schematic

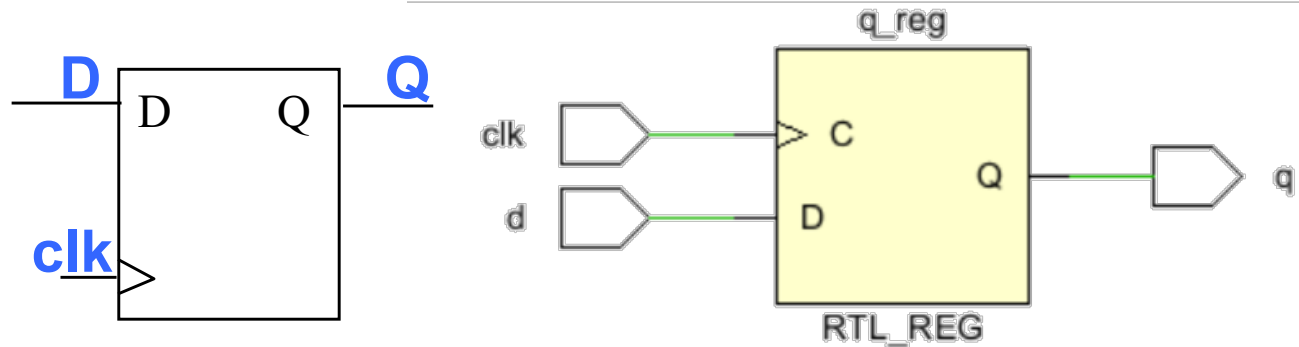


## Vivado Synthesized Schematic

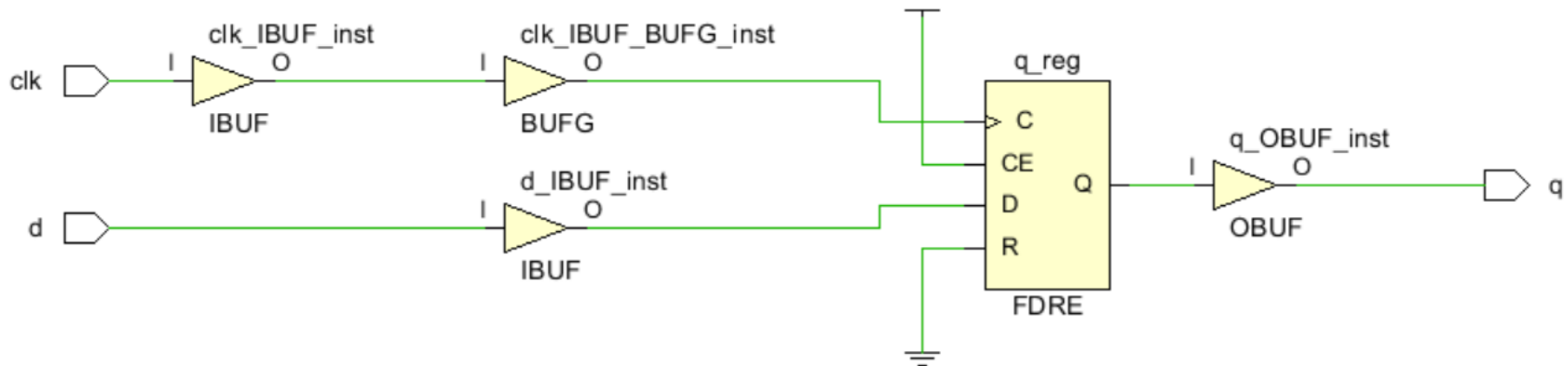


D Flip-Flop with Clock Enable and Synchronous Reset

# FDXX Primitives in 7series FPGA

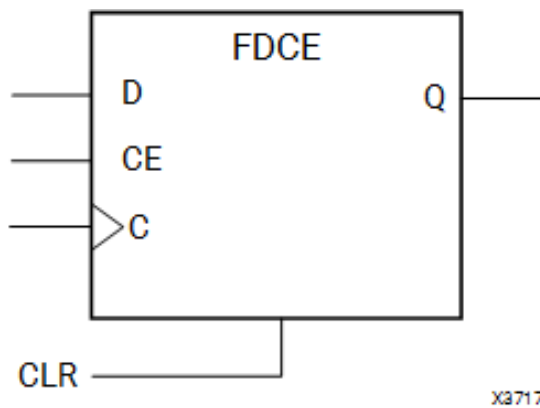
## 1 D Flip-Flop with Clock Enable and Asynchronous Reset



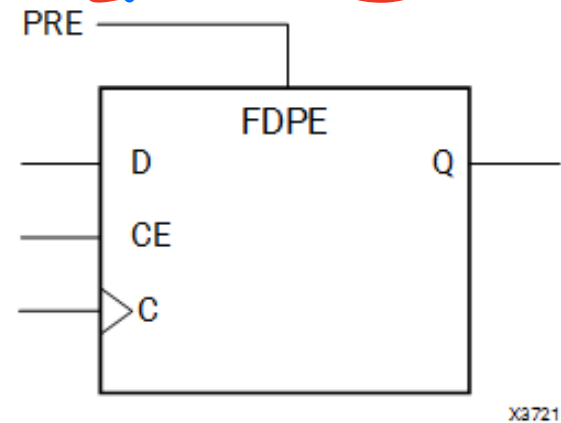
## 2 D Flip-Flop with Clock Enable and Asynchronous Set


 
## 3 D Flip-Flop with Clock Enable and Synchronous Reset


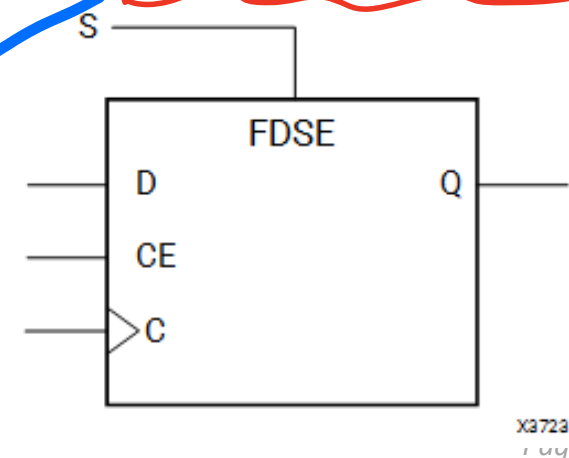
## 4 D Flip-Flop with Clock Enable and Synchronous Set






# Example - Practice Question

The 74'74B is an integrated circuit containing negative-edge triggered D flip-flops with synchronous set and asynchronous reset inputs. The D flip-flop receives four 1-bit input signals, D, CLK, S, CLR and produces two 1-bit output signals, Q and QB. Write a Verilog program that implements the D flip-flop according to the characteristic table shown below.

CLK	CLR	S	D	Q <sup>+</sup>
X	0	X	X	0
↓	1	0	X	1
↓	1	1	0	0
↓	1	1	1	1

Reset  
Set  
DFF

 

```
always @ ( neg edge CLK, neg edge CLR )
```

高有效 → posedge

低有效, 异步清零

# Practice Question

```
module dff ( input D, CLK, CLR, S, output reg Q, output QB );
```

```
always @ ( negedge CLK, negedge CLR )
```

```
begin
```

```
if ( CLR == 0 )
```

*Q <= 1'b0;*

```
else
```

*// CLR == 1*

```
begin
```

```
if ( S == 0 )
```

*Q <= 1'b1;*

```
else
```


*Q <= D;*

```
end
```

```
end
```

```
assign QB = ~Q;
```

```
endmodule
```

 


*Only "negedge CLK" is not enough*


CLK	CLR	S	D	Q <sup>+</sup>
X	0	X	X	0
↓	1	0	X	1
↓	1	1	0	0
↓	1	1	1	1

# D Flip-Flop... in Vivado?

## Vivado RTL Schematic

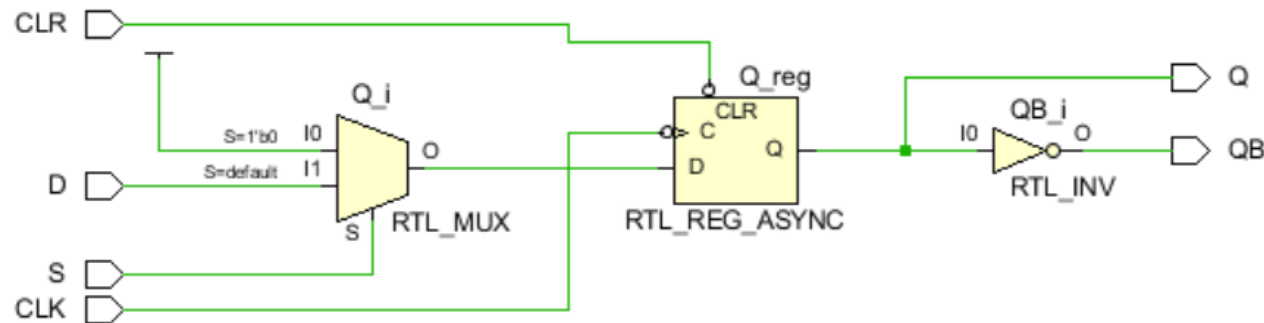

## Vivado Synthesized Schematic

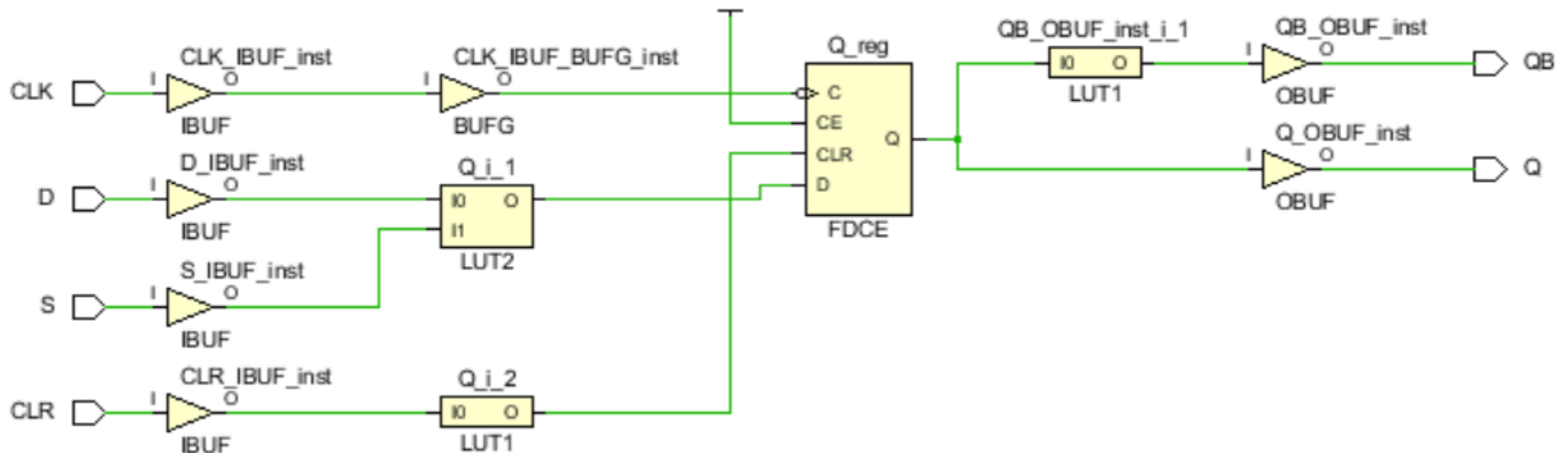

# Summary

---

- Operators ( $\sim$ ,  $*$ ,  $/$ ,  $+$ ,  $-$ ,  $\&$ ,  $^$ ,  $|$ )
- Continuous assignments (**assign**)
- Procedural assignments (**always**)
  - Blocking assignment (**=**)
  - Non-blocking assignment (**<=**)
- Modeling of multiple D Flip-flops
- Modeling of synchronous and asynchronous inputs