 


# **FSM : Finite State Machines**

---

# What is a FSM?

- **FSM** : Finite State Machine
- Synchronous Machine with “states” of operation
- At each *active clock edge*, combinational logic computes **outputs and next state**,  
as a function of **inputs and present state**




- Examples ?

# Mealy and Moore


- Moore: 输出写在“状态里面”
- Mealy: 输出写在“边 (transition) 上”
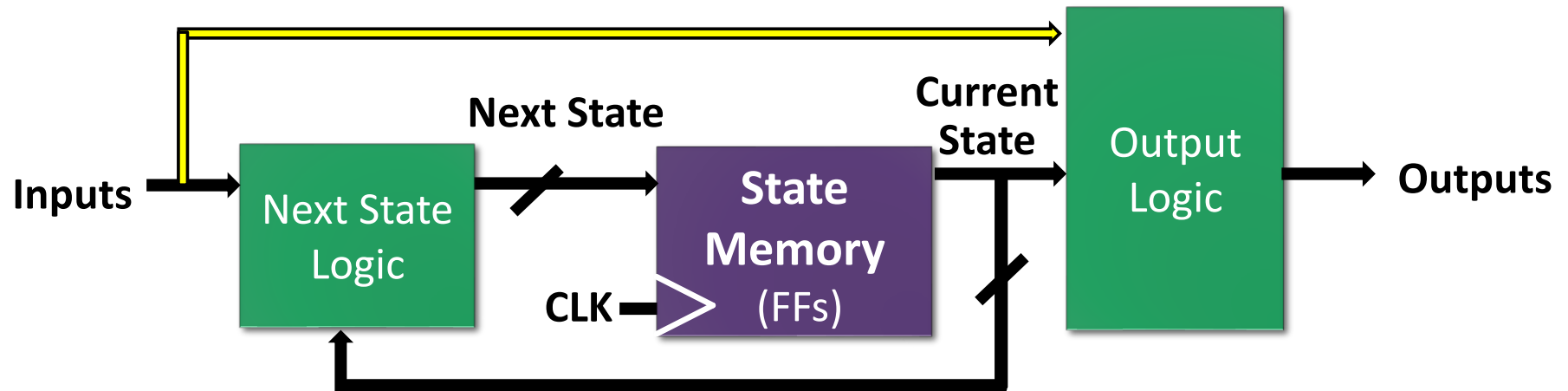
## Moore vs Mealy FSMs : Different Output Generation

- Mealy machine: *output is a function of a **present state & inputs**.*



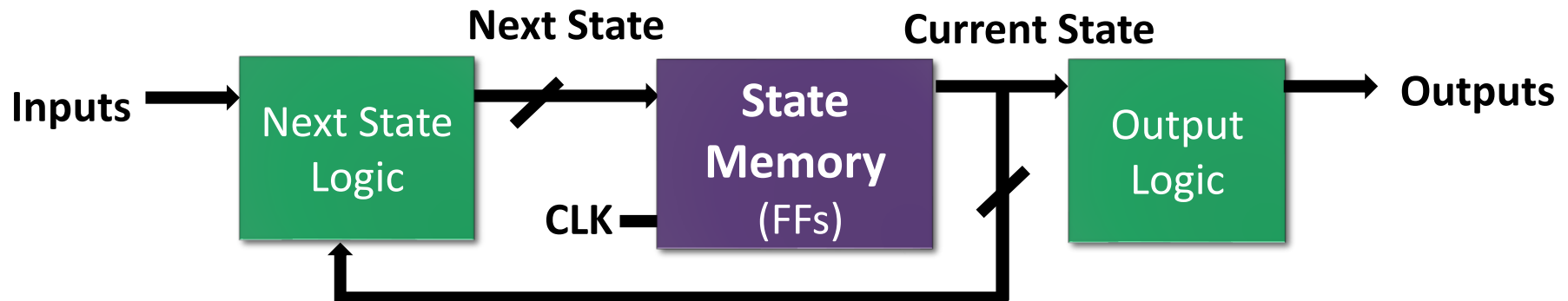- Moore machine: *output is a function of a **present state only**.*



# Structure

---

## State Memory

- set of  $n$  FFs store current state of machine; up to  $2^n$  states.
- FFs can be J-K or D, but D FFs simpler (1 input vs. 2 inputs for J-K FFs)

## Next State Logic

- combinational circuit which decides the next state of the machine based on current state and inputs:

$$\text{Next state} = f(\text{inputs}, \text{current state})$$

## Output logic


- combinational circuit which creates the output  
Moore : outputs depend on current state

$$\text{outputs} = g(\text{current state})$$

Mealy : outputs depend on the current state & inputs

$$\text{outputs} = g(\text{inputs}, \text{current state})$$

# Traffic Problem...

 

**At a busy intersection on campus...**

Students from the Law faculty are burying their heads in their books and are not looking where they are going.

Students from the Business faculty are occupied on their phones and aren't looking at where they're going either....


# Traffic Problem...



$L_B$



$T_B$

 


$T_L$



$L_L$



$L_L$

 

Avenue



$T_B$

$L_B$


Street

## Design a FSM to control the traffic lights!

- 1) Sensors  $T_B$  and  $T_L$  are TRUE when students are present. False otherwise.
- 2) Control traffic lights  $L_L$ ,  $L_B$  to be green, yellow, red.
- 3) Reset to Green on Law Ave and Red on Business St.
 
## Every 5 sec, check the traffic and decide what to do!

- If the lights on Business St. are green and there's no traffic, the lights turn yellow for 5 secs. After that, they turn red and Law Ave. lights turn green.
- So on, so forth.
- If there is traffic, lights do not change.





A SYSTEMATIC PROCEDURE TO GO FROM

IDEA  $\rightarrow$  IMPLEMENTATION




 
 
# Step 1 : State Transition Diagram

---


- Block Diagram of Desired System
- Design **State Transition Diagram** to represent FSM





     


# Moore State Transition Diagrams

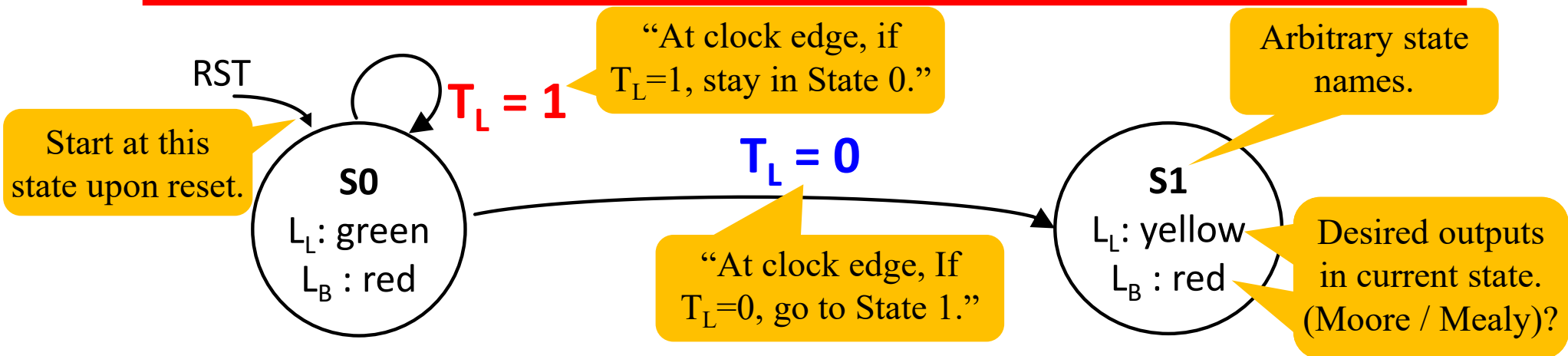




- Circles represent **states**.
  - \* Each state specifies values for all outputs (Moore)
- Arcs represent **transitions** between states.
  - \* **Labels** → input that triggers the transition.
  - \* Transitions take place on the **active edge** of the clock.
- Arc from outer space indicates initial state upon reset
- Within each state, for any combination of input values, there's exactly one applicable arc.

# Timing Diagram

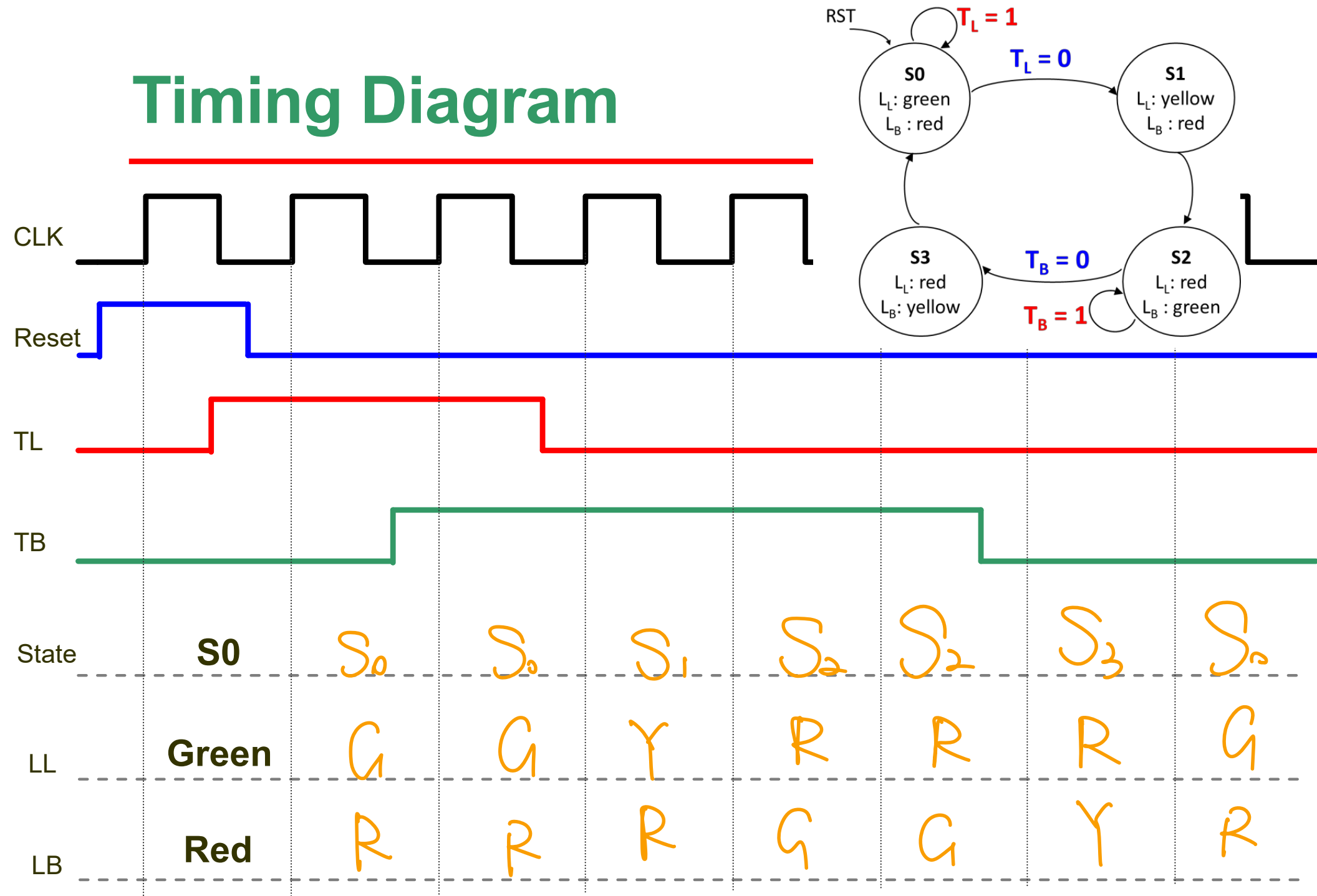
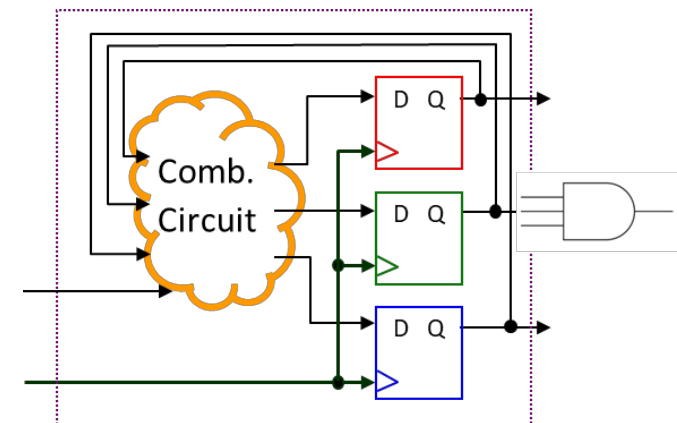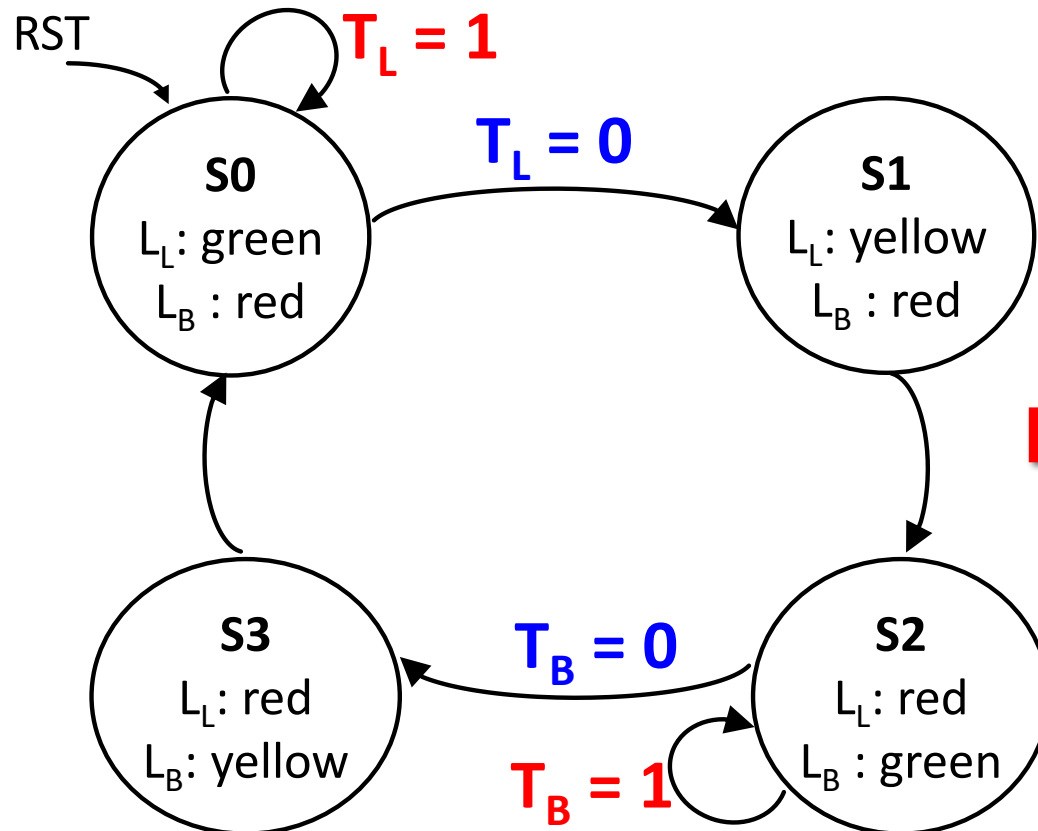 
# Step 1 : State Transition Diagram

- Block Diagram of Desired System
- Design **State Transition Diagram** to represent FSM



# Step 2 : Next State Table


1. From STD, find the number of states **4**
2. Number of bits / FFs required = **2** to go through these states
3. State Assignment

1. Sequential
2. One-hot (100,010,001)
3. Gray
4. Johnson
5. Output Encoded

State	$S_1S_0$
S0	00
S1	01
S2	10
S3	11

## 4. Next State Table

Current State	Inputs		Next State
S	$T_L$	$T_B$	S+
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

 

# Step 2 : Next State Table


## 5. State Generator Circuit

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_L$	$T_B$	$S_1^+$	$S_0^+$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

$$S_1^+ = \overline{S_1}S_0 + S_1\overline{S_0}T_B + S_1\overline{S_0}T_B$$

$$= S_1 \oplus S_0$$
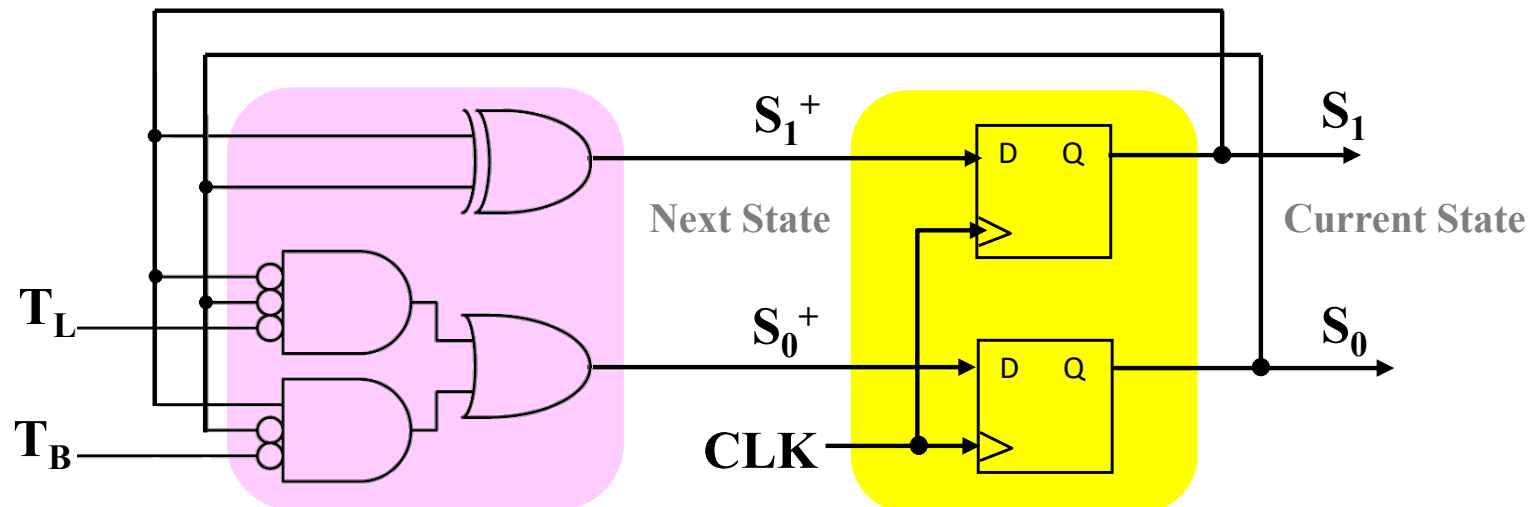
$$S_0^+ = \overline{S_1}\overline{S_0}T_L + S_1\overline{S_0}T_B$$



# Step 3 : Output Logic


## 1. Output Truth Table

Current State		Outputs			
$S_1$	$S_0$	$L_{L1}$	$L_{L0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1




Output	$L_1L_0$
Green	00
Yellow	01
Red	10

$$L_{L1} = S_1 \quad L_{L0} = \overline{S_1}S_0$$

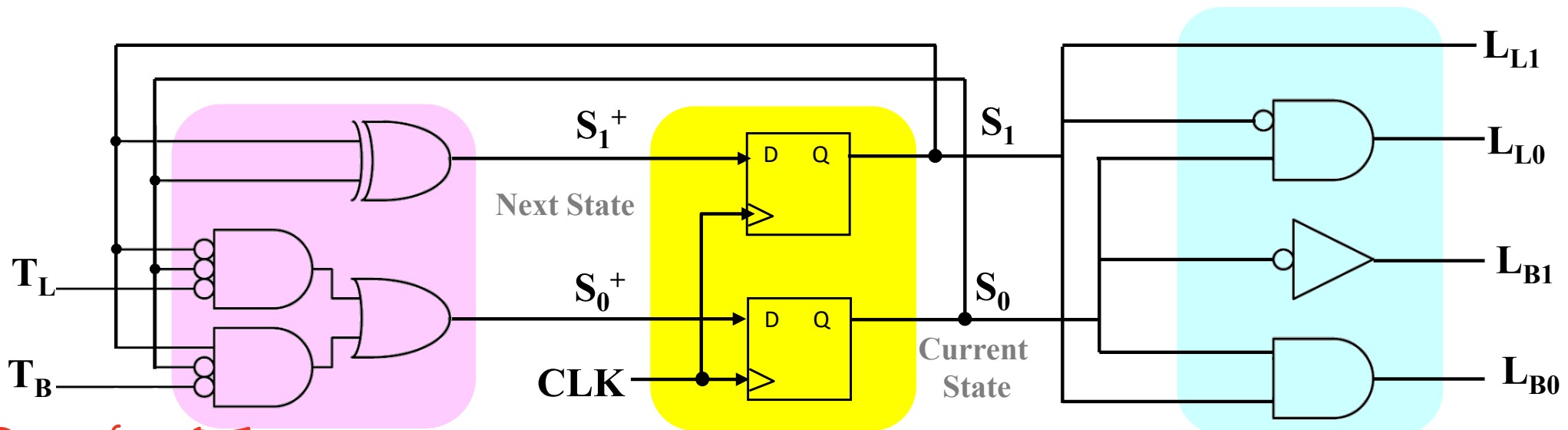
$$L_{B1} = \overline{S_1} \quad L_{B0} = S_1S_0$$




# Ta-Dah!

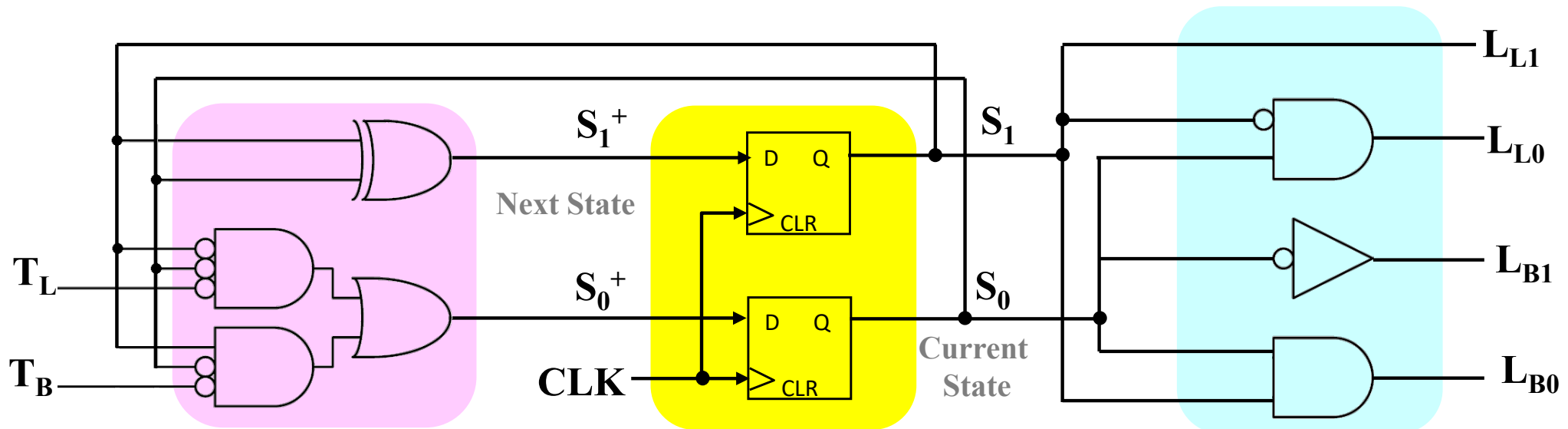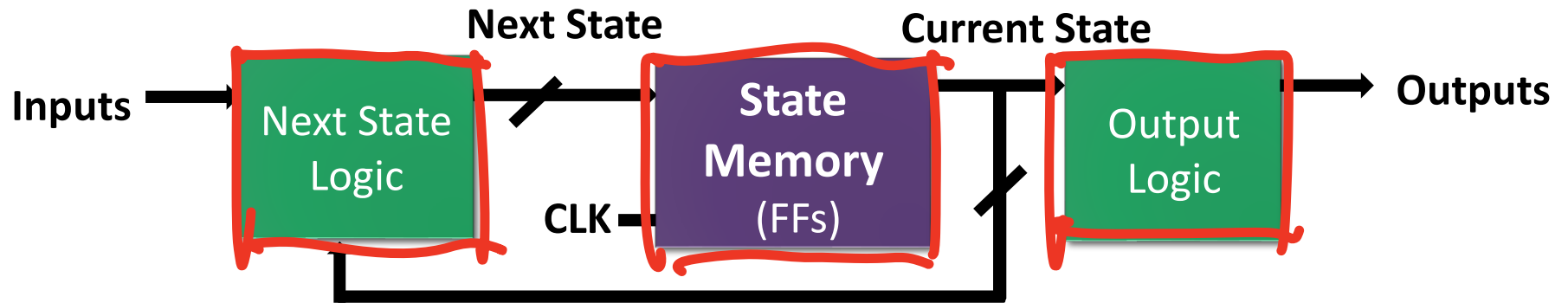 



 

# Verilog~! – Code Structure

 

**Combinational  
Circuit**



```
always @ (*)
```

**Sequential  
Circuit**




```
always @  
(posedge clk)
```

**Combinational  
Circuit**



```
assign y =
```

# FSM in Verilog

 

```
module fsm(input clk, ... , output ... );
  reg __ state, nextstate;
```

2个状态 (2 states) → 1 bit

```
parameter S0 = 2'b00;
parameter S1 = 2'b01;
```

**parameter** is used to define constants within a module, improving code readability.

```
always @ (*)
  case (state)
    S0 : nextstate = S1;
    S1 : nextstate = S0;
  endcase
```

**Next State Combinational Logic :**

(\*) code is triggered whenever any input changes → combinational logic.  
**case** represents next state table.

状态转移表 (State Transition Table)

```
always @ (posedge clk, posedge reset)
  if (reset) state <= S0;
  else      state <= nextstate;
```

**Sequential Logic :**

Use <= to infer flip-flops.  
*Is this Sync or Async reset?*

```
assign y = ( state == S0 );
```

**Output Logic :** Use **assign** to infer combinational logic.

```
endmodule
```

Equality Comparison :

a == b evaluates to 1 if a equals b.

## ① reg state, nextstate; (圈出来的地方)

### 含义 (逐字解释)

```
verilog

reg state, nextstate;
```

- **state**  
👉 当前状态 (存在寄存器里)
  - **nextstate**  
👉 组合逻辑算出来的“下一个状态”
  - **重难点 / 易错点**
  - state 和 nextstate 都是 **reg**
  - 因为：
    - state 在 时序 **always block** 里赋值
    - nextstate 在 组合 **always @(\*)** 里赋值
- FSM 中: state = 寄存器, nextstate = 组合信号

## ② parameter S0 = 2'b00; ...

### 含义

```
verilog

parameter S0 = 2'b00;
parameter S1 = 2'b01;
```

- 给状态编码起“名字”
- 提高可读性
- 不影响综合结果
- **考试常问**
- parameter ≠ 寄存器
- parameter 是编译期常量

## ③ 黄色块: Next State Combinational Logic

```
verilog

always @(*) begin
    case (state)
        S0: nextstate = S1;
        S1: nextstate = S0;
    endcase
end
```

**精确含义**

这是“下一状态逻辑”，纯组合逻辑

- always @(\*)  
👉 只要输入变，就重新算
- case(state)  
👉 就是“状态转移表”

- **重难点**
- 这是 组合逻辑
- ❌ 不能有 posedge
- ❌ 不能有“记忆”
- ❌ 不能漏 default (真实工程)

🔗 和状态转移图的关系

- 箭头 = case 里的分支
- 输入条件 = case 里的判断

## ④ 蓝色块: Sequential Logic (状态寄存器)

```
verilog

always @(posedge clk, posedge reset) begin
    if (reset)
        state <= S0;
    else
        state <= nextstate;
end
```

**精确含义**

这是 FSM 唯一的“存储部分”

- posedge clk  
👉 同步 FSM
- posedge reset  
👉 异步复位 (Async reset)

## 🔴 考试必考点

? Is this Sync or Async reset?

✓ Async reset

📌 判断规则 (直接背):

- reset 在 sensitivity list 里 → 异步
- reset 在 if、但不在 list 里 → 同步

## ⑤ 粉色块: Output Logic (Moore)

verilog

```
assign y = (state == S0);
```

## 精确含义

输出只由当前状态决定

🔴 这是 Moore 的铁证

- 输出:
  - ❌ 不看输入
  - ✅ 只看 state

📌 如果是 Mealy:

- 输出逻辑里一定会出现 输入信号

## 三、这页在“暗考”你什么?

🔥 考点 1: FSM 的三段式结构 (必背)

部分	写法
Next State Logic	always @(*)
State Register	always @(posedge clk ...)
Output Logic	assign/always @(*)

🔥 考点 2: RTL 思维

这页就是教你什么叫 RTL:

寄存器 + 数据如何在时钟下流动

🔥 考点 3: 为什么不用一个 always 写完?

因为:

- 会混合组合 + 时序
- 容易 latch
- 不是标准 RTL FSM

## 四、一句话终极总结 (考试用)

FSM 的 Verilog 标准模板 =  
一个 always @(\*) 算 nextstate,  
一个 always @(posedge clk) 存 state,  
一个 assign/always 生成输出。

# FSM Traffic Controller in Verilog

```
module traffic (input clk, reset,
TL, TB, output [1:0] LL, LB);

reg [1:0] state, nextstate;

parameter S0 = 2'b00, S1 = 2'b01,
S2 = 2'b10, S3 = 2'b11;

parameter green = 2'b00,
yellow= 2'b01, red= 2'b10;

always @ (*) begin
    case (state)
        S0: nextstate = TL ? S0 : S1;
        S1: nextstate = S2;
        S2: nextstate = TB ? S2 : S3;
        S3: nextstate = S0;
    endcase
end
```

👉 答案是:

两种写法都生成组合逻辑，功能等价，只是表达方式不同

- 一个是 位运算/编码技巧
- 一个是 条件判断/可读性高


```
always@(posedge clk, posedge reset)
begin
    if (reset) state <= S0;
    else state <= nextstate;
end

//What's the diff between these
//2 ways of coding output logic ?

assign LL
= {state[1], ~state[1] & state[0]};

assign LB =
(state== S0 || state== S1) ? red :
( (state == S2) ? green : yellow );



endmodule
```

 

# Traffic Controller

- Check the waveforms in the timing diagram below...


Are they correct?

 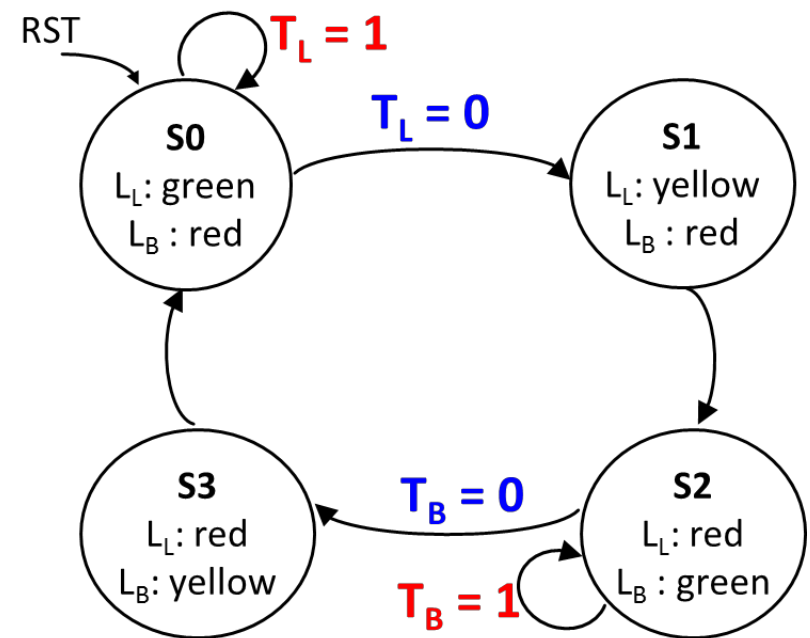

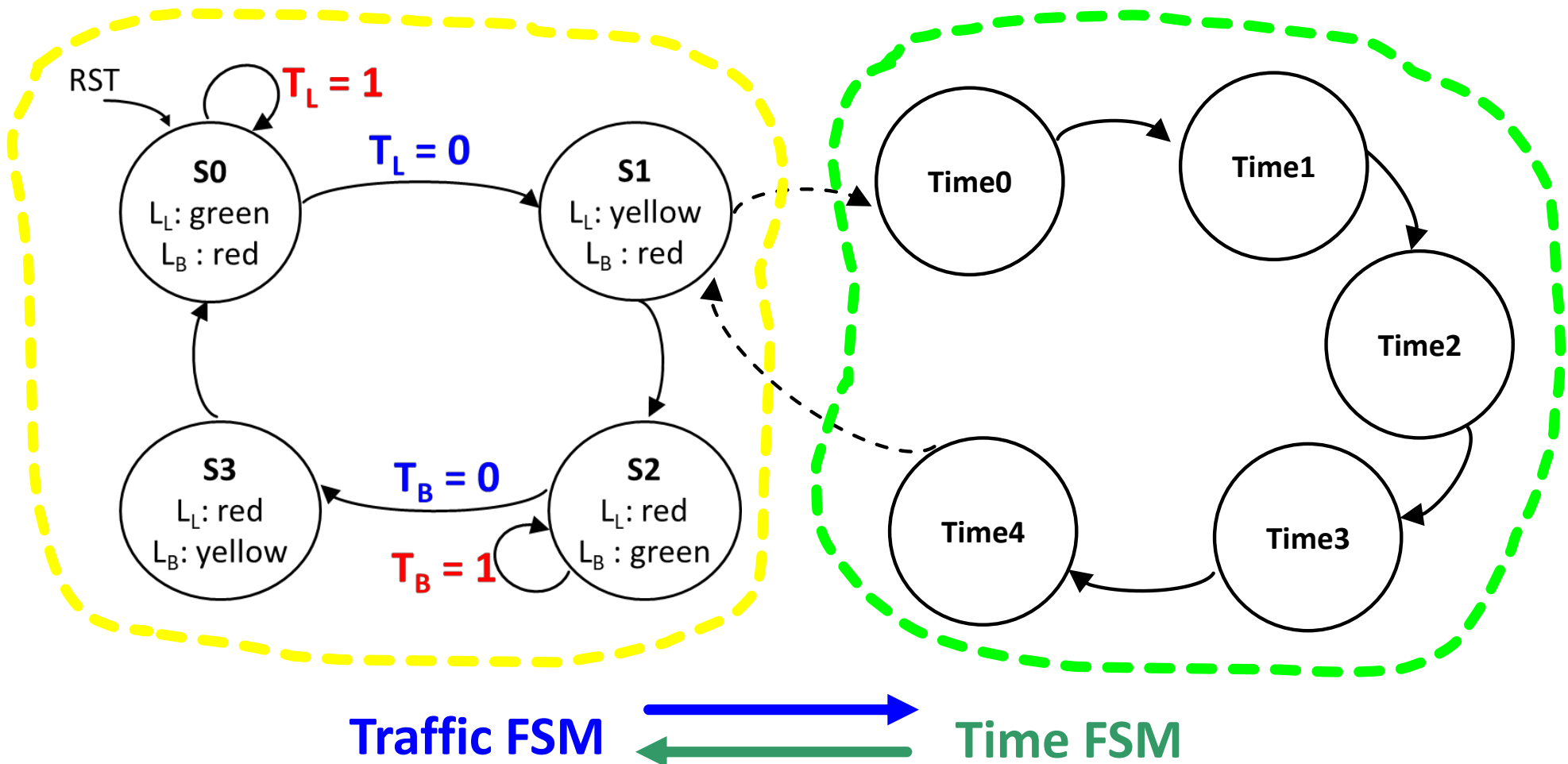
# Modular Design of FSMs

What if we want to stay in state S1 for five clock cycles?

Designing complex FSMs is often easier if they can be broken down into simpler FSMs that interact.



# Modular Design of State Machines

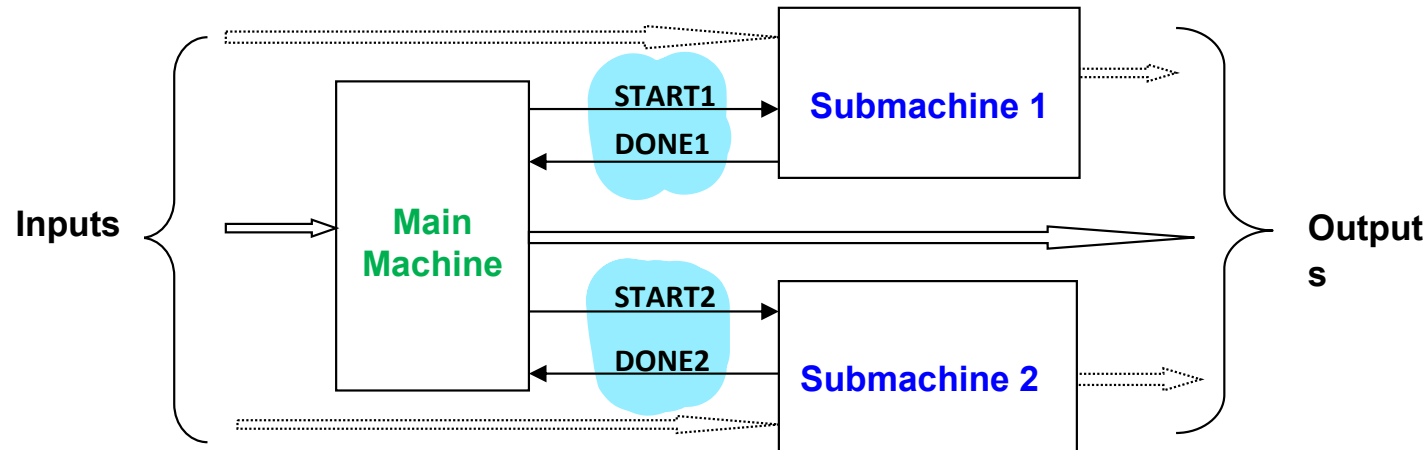



- **Main machine** : executes main algorithm, controls the **submachines** & get the job done. Commands & gets feedback signals from **submachines**.
- **Submachines** respond to external inputs & commands from **main machine**. Can give outputs as well as feedback to the **main machine**.
- Common examples of **submachines** are **counters**, **shift registers**, etc.
- Sometimes the **main machine** is called the **controller** and the **submachines** are called **controlled circuit elements** or **architectural elements**.
- **Trick here** is to **modularize** appropriately, and pick suitable components for the submachines that simplify the design problem.




# Modularizing...



---




What is a natural submachine we can use?

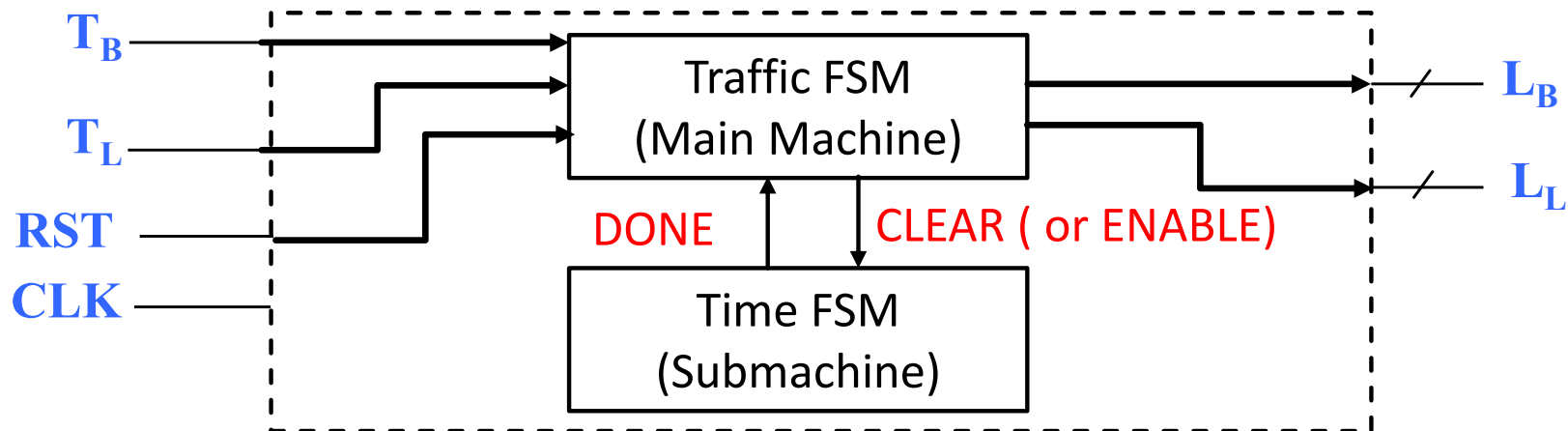 

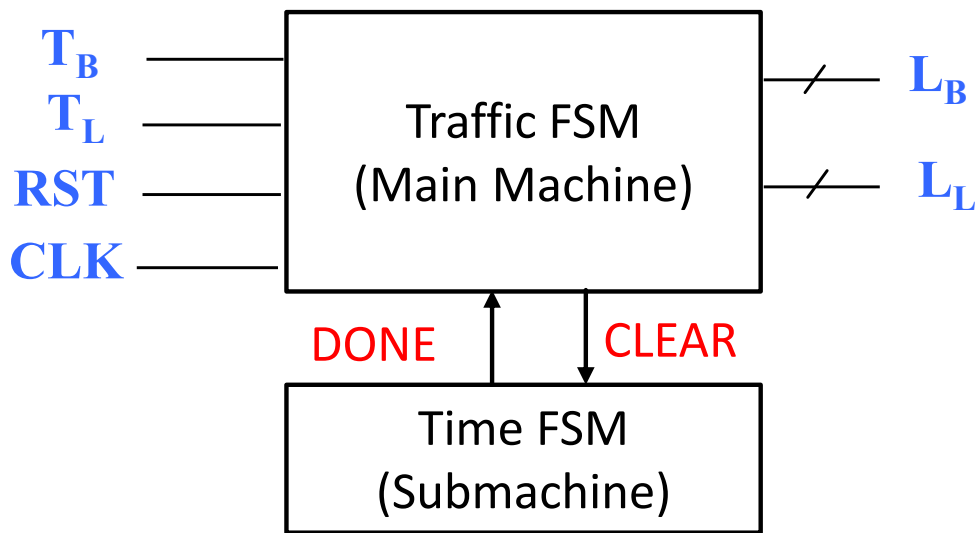


clear=1

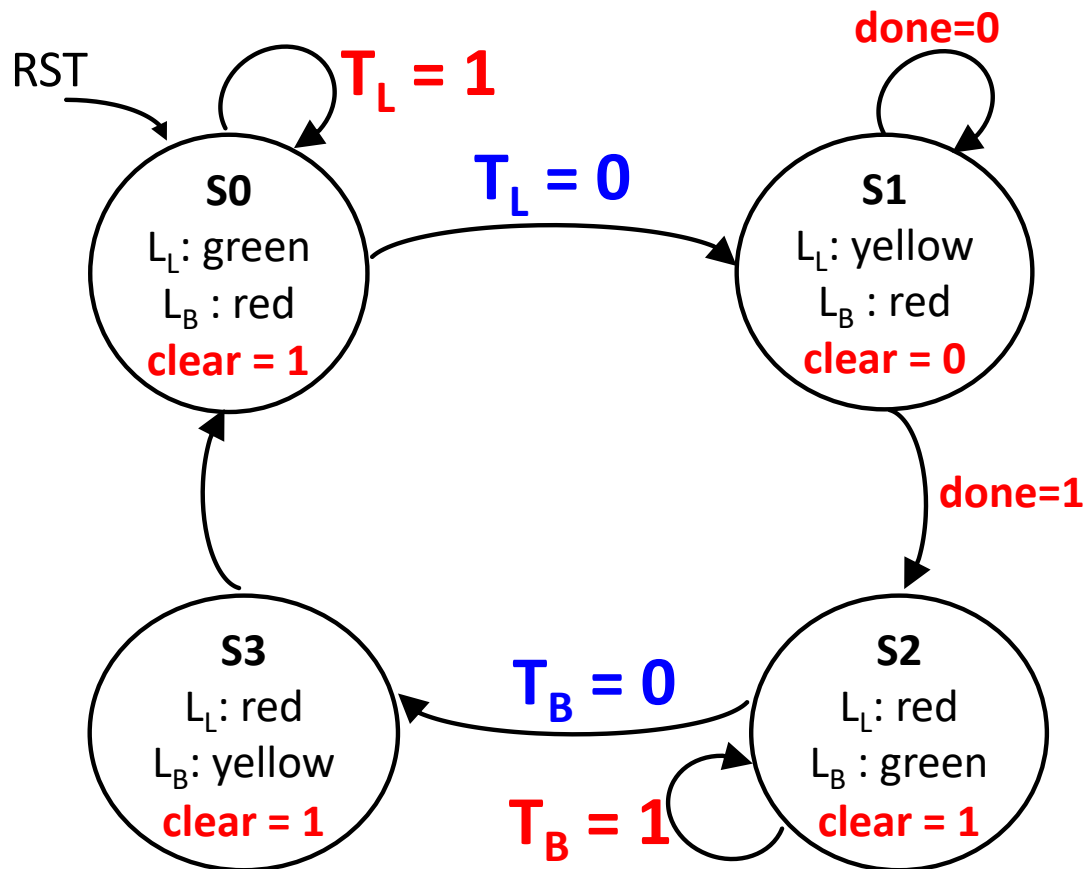 

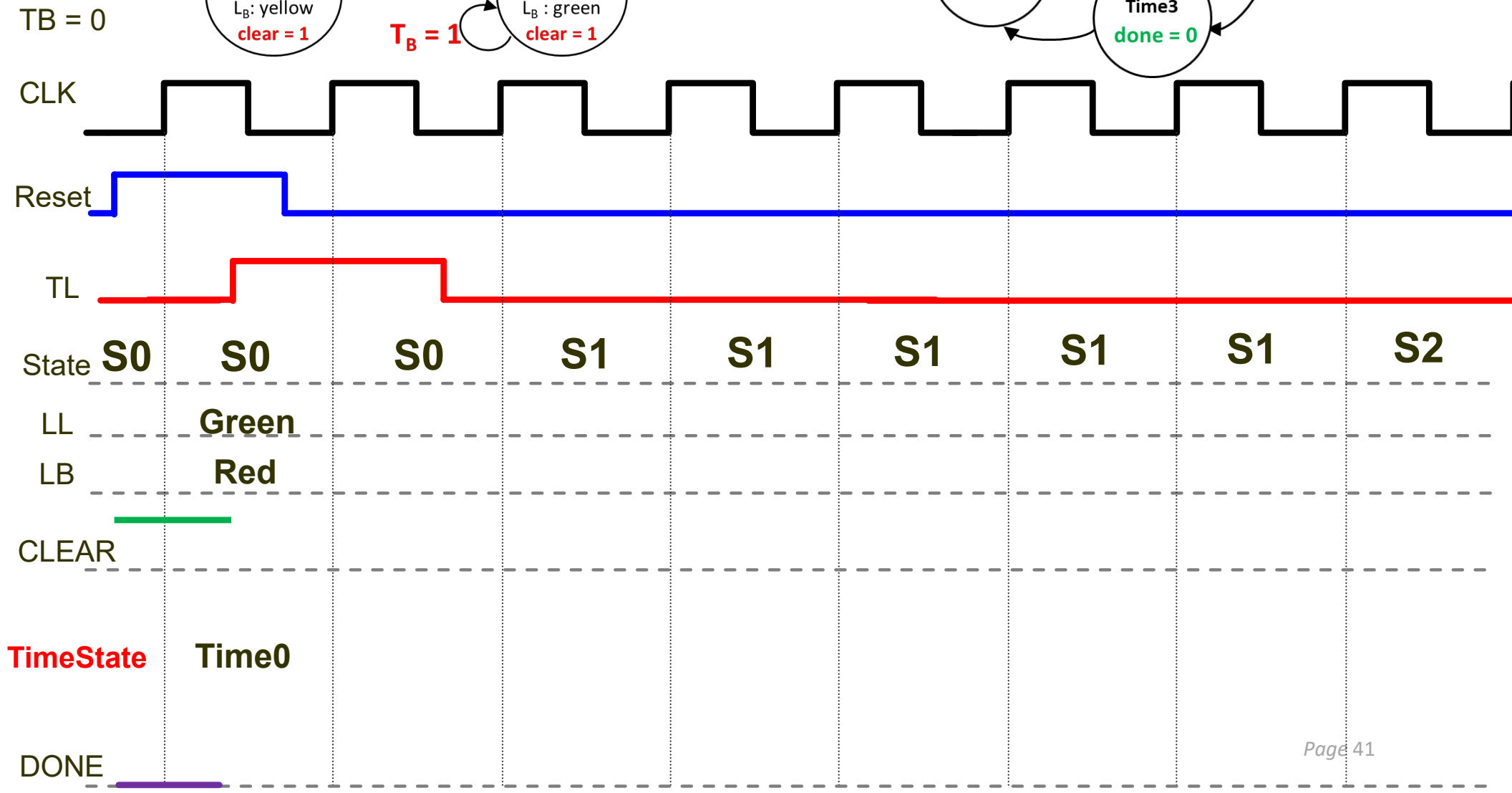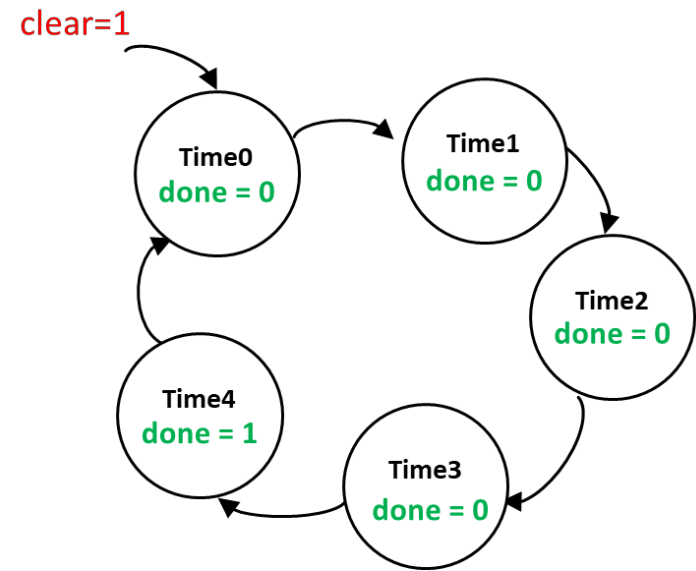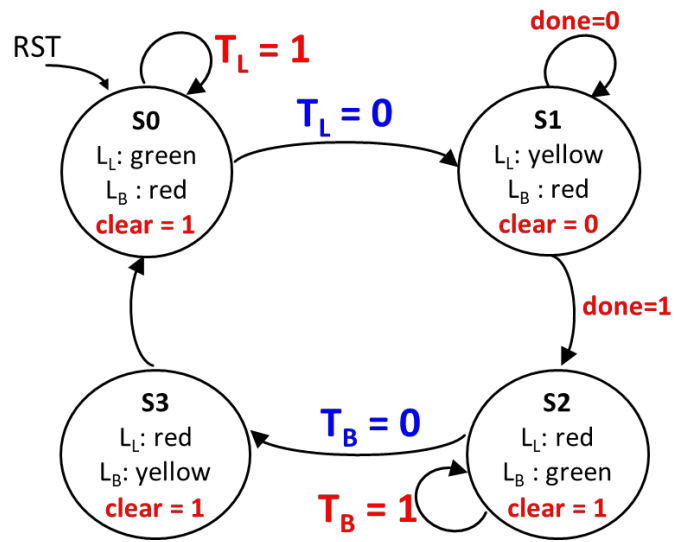

# FSM with Submachine

 

```

module traffic (input clk, reset,
TL, TB, output [1:0] LL, LB);

reg [1:0] state, nextstate;
wire clear, done;

parameter S0 = 2'b00, S1 = 2'b01,
S2 = 2'b10, S3 = 2'b11;

parameter green = 2'b00,
yellow= 2'b01, red= 2'b10;

always @ (*) begin
    case (state)
        S0: nextstate = TL ? S0 : S1;
        S1: nextstate = done? S2 : S1;
        S2: nextstate = TB ? S2 : S3;
        S3: nextstate = S0;
    endcase
end

always@(posedge clk, posedge
reset) begin
    if (reset) state <= S0;
    else state <= nextstate;
end

```

```

assign LL
= {state[1], ~state[1] & state[0]};

```

```

assign LB =
(state== S0 || state== S1) ? red :
( (state == S2) ? green : yellow );
-----

```

```

assign clear = (state != S1);

```

```

reg [2:0] count = 3'b000;

```

```

always @(posedge clk) begin

```

```

    if (clear) count <= 0;

```

```

    else begin

```

```

        count <= (count == 3'b100) ? 0 : count + 1;

```

```

    end

```

```

end

```

```

assign done = (count == 3'b100);

```


```

endmodule

```

0~4

# Vivado : fsm\_extraction

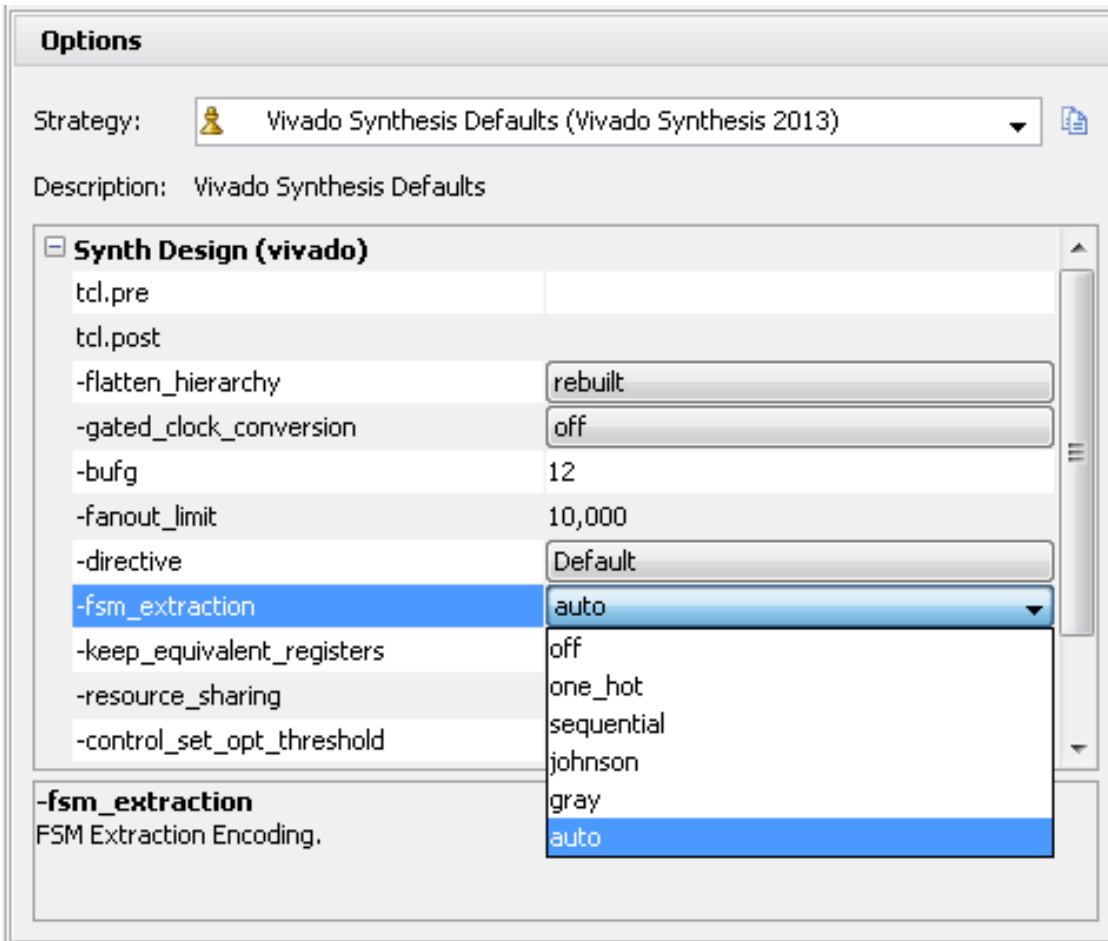

- INFERENCE of FSMs in Vivado
- Built-in FSM encoding strategies to for optimization

## Possible Encoding Strategies :

- Auto
- One-Hot
- Gray State 只变一位
- Johnson State 环形移位编码器
- Sequential State 顺序

[https://www.xilinx.com/support/documentation/sw\\_manuals/xilinx2017\\_1/ug901-vivado-synthesis.pdf](https://www.xilinx.com/support/documentation/sw_manuals/xilinx2017_1/ug901-vivado-synthesis.pdf)

What is FSM inference in Vivado?

✓ 答:

Vivado can automatically recognize FSM structures from RTL and optimize them using built-in encoding strategies.

Which FSM encoding is most suitable for FPGA?

✓ 答:

One-hot encoding, due to fast decoding and abundant flip-flops.

Does user-defined state encoding force Vivado to use that encoding?

✓ 答:

No. Vivado may re-encode states internally unless constrained.

## 八、一句话终极总结（直接背）

**Vivado 会自动识别 FSM，并根据设计目标选择合适的状态编码；  
在 FPGA 中，One-Hot 是最常见的优化选择。**